



Indian Institute of Technology, Kanpur
Department of Electrical Engineering

ESC 201A

Midterm Examination
Saturday, 26th Feb, 2022

1 Use Thevenin's theorem to determine Z_L such that maximum power is dissipated in the load impedance Z_L . Determine also the average power dissipated in Z_L and the average power supplied by each source.

(5 marks)

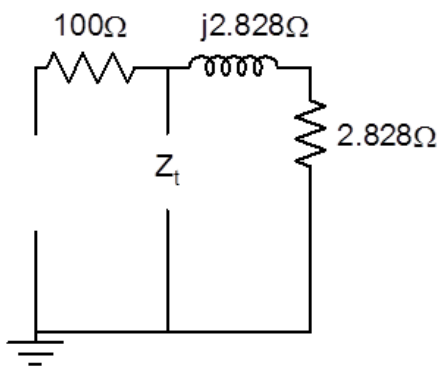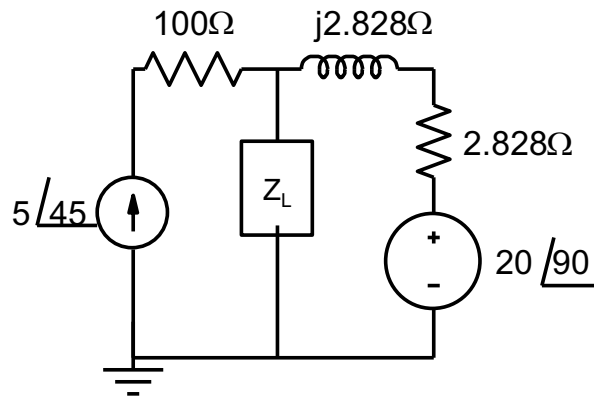


Solution: Thevenin's impedance can be found from the equivalent circuit

$$Z_t = 2.82 + j2.82 = 4\angle 45^\circ \quad [1 \text{ mark}]$$

For maximum power transfer, we should choose:

$$Z_L = \bar{Z}_t = 2.82 - j2.82 = 4\angle -45^\circ \quad [1 \text{ mark}]$$

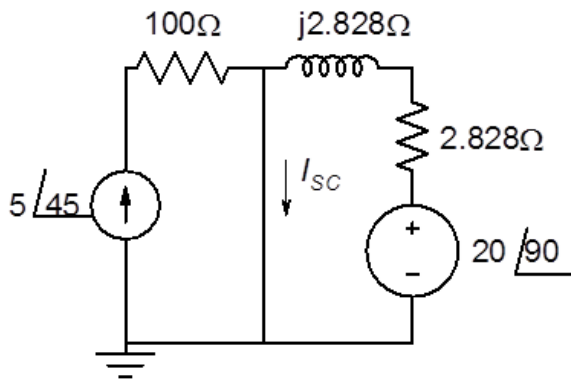Thevenin's voltage can be found by first finding the short circuit current:



$$I_{sc} = 5\angle 45^\circ + \frac{20\angle 90^\circ}{2.82 + j2.82} = 10\angle 45^\circ$$

$$V_t = I_{sc} * Z_t = 10\angle 45^\circ * 4\angle 45^\circ = 40\angle 90^\circ$$

[1 mark]


Current through load:

$$I_L = \frac{40\angle 90^\circ}{4\angle 45^\circ + 4\angle -45^\circ} = j5\sqrt{2}$$

$$\operatorname{Re}(Z_L) = R_L = 4 \cos(-45^\circ) = \frac{4}{\sqrt{2}}$$

$$P_L = \frac{(5\sqrt{2})^2 R_L}{2} = 70.1W \text{ [2 mark]}$$

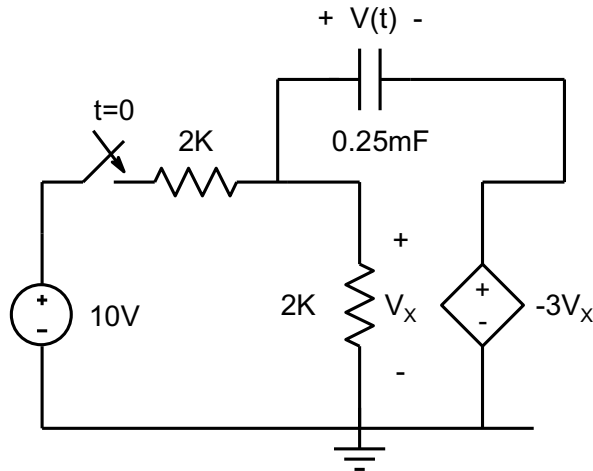2. Assuming that the capacitor does not have any initial charge, determine the voltage across the capacitor $V(t)$ as a function of time after the switch is closed at $t = 0$. **(5 marks)**



Solution:

$$v(t) = v(\infty) + \{v(0^+) - v(\infty)\}e^{-t/\tau}$$

$$v(0^+) = 0 \quad [1 \text{ mark}]$$


At $t \rightarrow \infty$, the capacitor is open circuit. Therefore,

$$v_X = \frac{2K}{2K + 2K} * 10 = 5V$$

$$v(\infty) = V_X - (-3V_X) = 4V_X = 20V \quad [1 \text{ mark}]$$

$$\tau = CR_{eq}$$

R_{eq} can be found from the circuit:

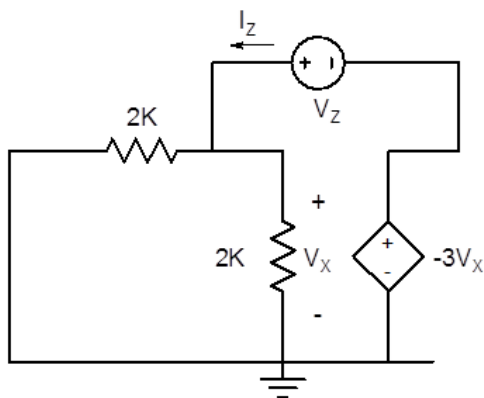

$$R_{eq} = \frac{v_Z}{i_Z}$$

$$v_Z = v_X - (-3v_X) = 4v_X$$

$$i_Z = \frac{v_X}{1K}$$


$$R_{eq} = \frac{v_Z}{i_Z} = 4K \quad [1 \text{ mark}]$$

$$\tau = CR_{eq} = 1s \quad [1 \text{ mark}]$$


$$v(t) = 20\{1 - e^{-t}\} \quad [1 \text{ mark}]$$

3. Design a diode circuit to convert the triangular waveform into a trapezoidal waveform as shown below. Give the circuit diagram along with typical component values, and give an explanation for your choice of components. Assume ideal diodes with cut-in voltage of zero volts.

(5 marks)

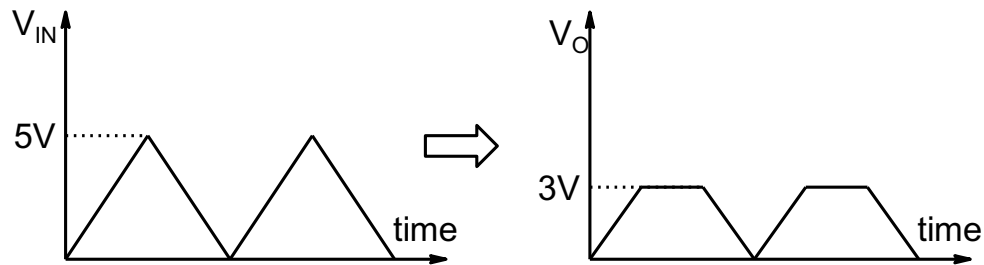

Solution:

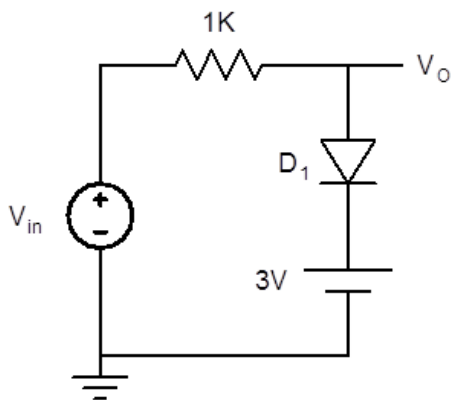

For input voltage less than 3V, diode is OFF so $V_O = V_{in}$. For larger input voltage, the diode turns on and acts like a short circuit. Thus, $V_O = 3V$. [2 marks]

circuit: [3 marks] (1 mark per component)

4 An amplifier has a transfer function of the form:


$$G(\omega) = \frac{V_O(\omega)}{V_{in}(\omega)} = \frac{100 \times j(\omega/\omega_L)}{\{1 + j(\omega/\omega_L)\}\{1 + j(\omega/\omega_H)\}}$$

Sketch Bode plot of the transfer function and determine suitable values for corner frequencies such that amplifier can amplify audio frequencies in the range 20-20KHz equally well. **(5 marks)**

Solution:

$$20 \log_{10}(|G(\omega)|) = 40 + 20 \log_{10}\left(\frac{\omega}{\omega_L}\right) - 10 \log_{10}\left(1 + \left(\frac{\omega}{\omega_L}\right)^2\right) - 10 \log_{10}\left(1 + \left(\frac{\omega}{\omega_H}\right)^2\right)$$

$$H_0 = 40 \text{ dB}$$

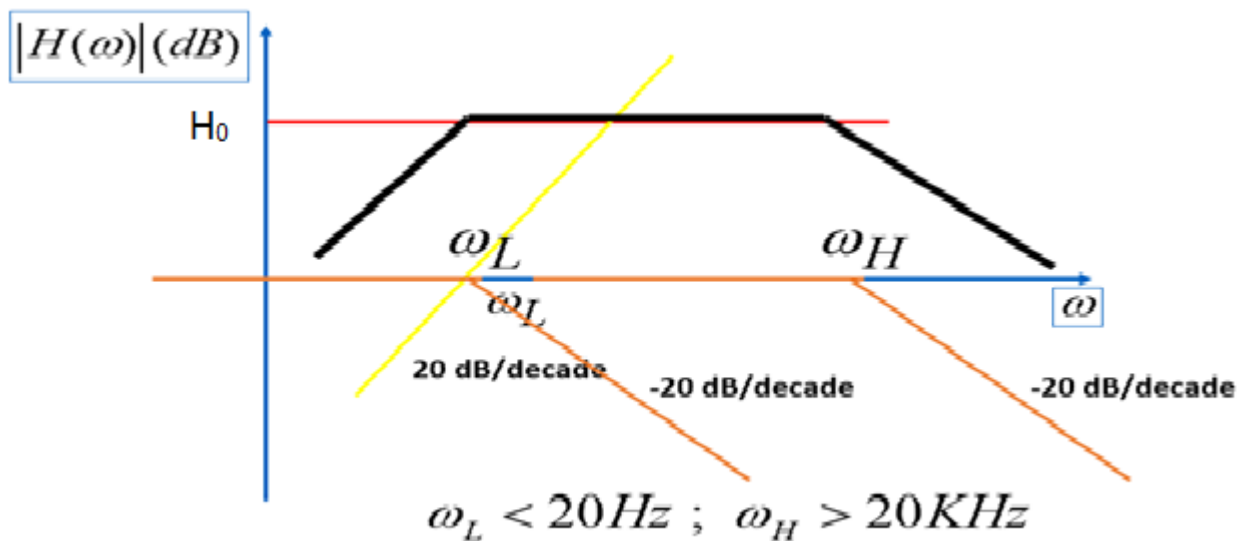

Plot: **[3 marks]**

ω_L, ω_H : **[1 + 1 = 2 marks]**