

Q(a) For a modulo-6 counter $2^N \geq 6$ required & $N \geq 3$, so 3 FFs required.

1/4 for each row correct to add up to 2

ck pulse	Q_{2n}	Q_{1n}	Q_{0n}	Q_{2n+1}	Q_{1n+1}	Q_{0n+1}	J_2	K_2	J_1 , K_1	J_0 , K_0
1	0	0	0	0	0	0	1	0	0, X	0, X
2	0	0	1	0	0	1	0	0	1, X	1, X
3	0	1	0	0	1	1	0	0	X, 0	1, X
4	0	1	1	1	0	0	1	X, 0	X, 1	X, 1
5	1	0	0	1	0	1	0	X, 0	0, X	1, X
6	1	0	1	0	0	0	X	1	0, X	X, 1
	0	0	0	0	0	1				

JK Table

Q_n	Q_{n+1}	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Q_{2n}	Q_{2n+1}	$J_1 = \bar{Q}_2 Q_0$	$1/2$
0	0	0, X, *, 0	
1	0	(1, X), *, 0	

$$\frac{1}{2} J_0 = 1$$


$$\frac{1}{2} K_0 = 1$$

X is Don't care
* is Unused.


$$J_2 = Q_1 Q_0 \quad \frac{1}{2}$$

Q_{2n}	Q_{2n+1}	$J_2 = Q_1 Q_0$	$1/2$
0	0	0, 0, *, X	
1	0	(1, *), X	

Q_{2n}	Q_{2n+1}	$K_2 = Q_0$	$1/2$
0	0	X, X, *, 0	
1	0	(X, X), *	

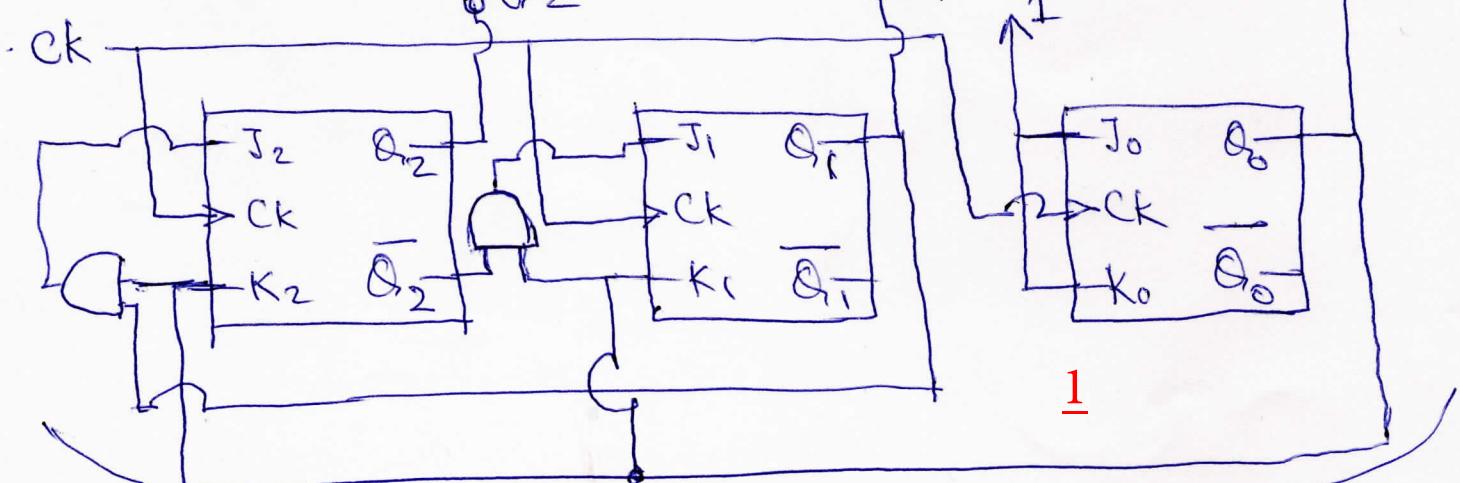

Q(b)

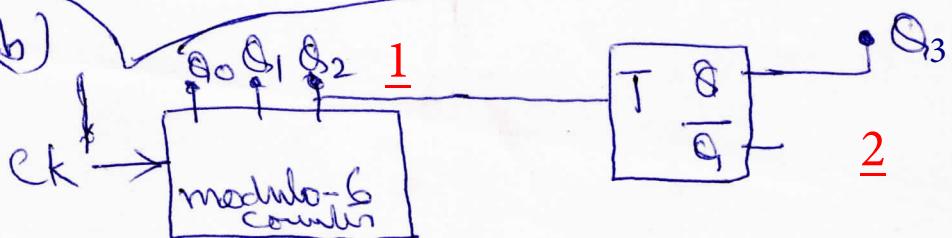

(Q.7.

Truth Table required.

No.	A	B	C	D	a	b	c	d	e	f	g	\overline{a}	\overline{b}
$\rightarrow 0$	0	0	0	0	1	1	1	1	1	1	0	1	0
$\rightarrow 1$	0	0	0	1	1	1	1	1	0	0	0	1	1
$\rightarrow 2$	0	0	1	0	1	1	1	1	0	0	0	1	1
$\rightarrow 3$	0	0	1	1	1	1	1	1	0	0	1	1	1
$\rightarrow 4$	0	1	0	0	1	1	1	1	0	0	0	1	1
$\rightarrow 5$	0	1	0	1	1	1	1	1	0	0	0	1	1
$\rightarrow 6$	0	1	1	0	1	1	1	1	1	0	0	1	1
$\rightarrow 7$	0	1	1	1	1	1	1	1	0	0	0	1	1
$\rightarrow 8$	1	0	0	0	1	1	1	1	1	1	1	0	1
$\rightarrow 9$	1	0	0	1	1	1	1	1	0	0	1	1	1

All other combinations do not appear & therefore are
Don't Cares. *

$\therefore a = b = c = 1$ always. 1

Minimizing d, e, f, and g.

(d)

AB	00	01	11	10
CD	00	1	*	1
01	1	*	0	
11	1	0	*	*
10	1	*	*	

$$d = \bar{D} + \bar{A}\bar{B} + \bar{A}\bar{C}$$

(e)

AB	00	01	11	10
CD	00	1	*	1
01	0	0	*	0
11	0	0	*	*
10	0	0	*	*

$$e = \bar{B}\bar{C}\bar{D}$$

(f)

AB	00	01	11	10
CD	00	1	*	1
01	0	0	*	1
11	0	0	*	*
10	0	0	*	*

$$f = \bar{B}\bar{C}\bar{D} + A$$

AB	00	01	11	10
CD	00	1	*	1
01	0	0	*	1
11	1	0	*	*
10	0	0	*	*

$$g = A + \bar{B}CD$$

$$d = \bar{D} + \bar{A}\bar{B} + \bar{A}\bar{C} \quad (1/2 + 1/2 + 1/2 = 1.5)$$

$$e = \bar{B}\bar{C}\bar{D} \quad 1$$


$$f = A + \bar{B}\bar{C}\bar{D} \quad (1 + 1/2) = 1.5$$

$$g = A + \bar{B}CD.$$

$$1 \quad 1/2$$

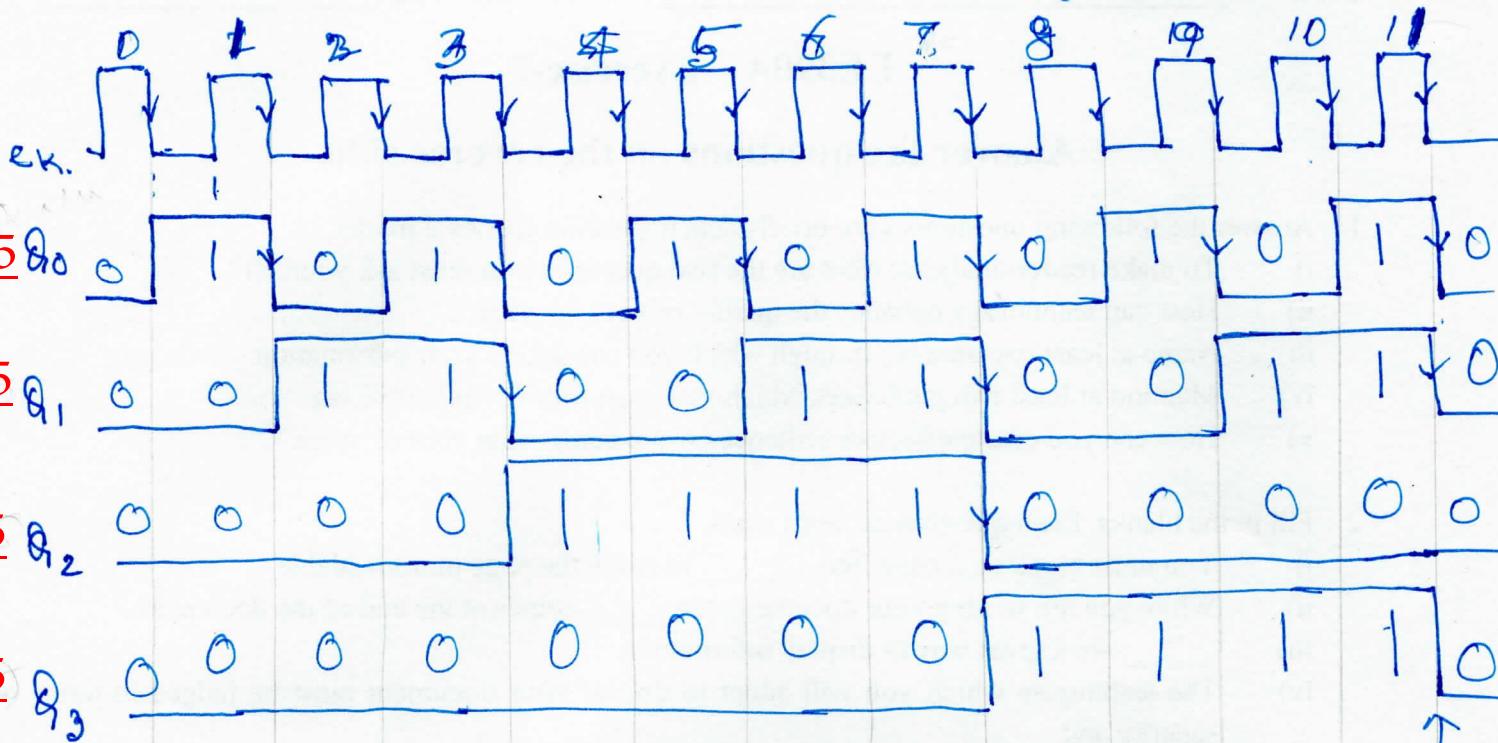6)

Assume 0, 0, 0, 0 at start. $\therefore P_r = 1, C_r = 1$.
No change.



The And gate will be on when Q_3, Q_1, Q_0 are all 1's and $C_r = 0, P_r = 1$ at this time which will reset the FFs to 0, 0, 0, 0. 1

11 clock pulses have lapsed before the state comes back to 0, 0, 0 again and the counter counts from 0000 to 1011.

$$\therefore N = 11. \text{ (Count of 11). } \rightarrow (1011)_2 = (11)_{10}.$$

If one looks at the connection and can figure out that the NAND gate will only turn on when the output is 1011, which amounts to a count of 11, then directly 4 marks should be given. However, as the question asks for the sketch the rest of the point cannot be awarded. If one also shows that the Cr input sets it back to 0, 0, 0, 0 then another 1 mark should be given.

Can be seen from the $C_r = 0$ for the NAND gate.

So if this justification is given with the answer "11" gets 4 pts without doing any sketch.


85.125

5)	2 85	
	2 42 → 1 LSB	
	2 21 → 0	
	2 10 → 1	
	2 5 → 0	
	2 1 → 1	
	2 0 → 0	binary point
	0 → MSB	1/2

1/2

$$\begin{aligned}
 & \text{MSB} & 0.125 \times 2 \\
 & 0 \leftarrow 0.250 \times 2 \\
 & 0 \leftarrow 0.500 \times 2 \\
 & 1 \leftarrow 1.0 \\
 & \text{LSB.} \\
 & & 1/2
 \end{aligned}$$

Register A

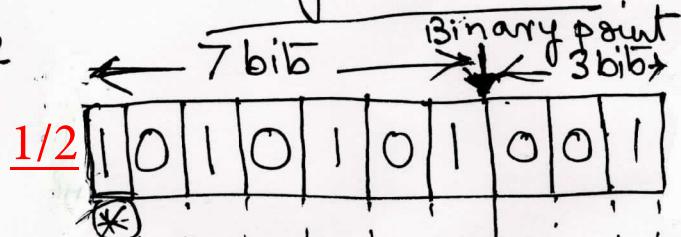

1/2

	32.5	
2	32	LSB
2	16 → 0.	
2	8 → 0	
2	4 → 0	
2	2 → 0	
2	1 → 0	MSB
	0 → 1	Binary point

1/2

1/2 can be given in either (a) or (b). This 1/2 should be there somewhere out of 7

∴ A > B. ∴ Need to take
1' compliment of B

Add 2' compliment of B
add 1 for Register C

1/2

0:	1	0	0	0	0	0	1	0	0
----	---	---	---	---	---	---	---	---	---

Register B

In this case comparison
is easy. Can be done
by checking only
the MSB of the 2 numbers.

1	0	1	1	1	1	1	0	1	1
---	---	---	---	---	---	---	---	---	---

1/2

1	0	1	1	1	1	1	1	1	0	0
---	---	---	---	---	---	---	---	---	---	---

1

Sum Registers A & C
4 store in D register.

[A]	1	0	1	0	1	0	0	1
-----	---	---	---	---	---	---	---	---

[C]	1	0	1	1	1	1	1	0	0
-----	---	---	---	---	---	---	---	---	---

1 [D]	0	1	1	0	1	0	0	1	0
-------	---	---	---	---	---	---	---	---	---

Reject overflow

$$\begin{aligned}
 & \text{Check: } 85.125 - 32.5 = 52.625 \\
 & D = 2^5 + 2^4 + 2^2 + 2^{-1} + 2^{-3} \\
 & = 32 + 16 + 4 + 0.5 + 0.125 = 52.625
 \end{aligned}$$

gets 1/2 Extra for showing this

B ⇒	0	1	0	0	0	0	0	1	0	0
-----	---	---	---	---	---	---	---	---	---	---

1/2

X 1/2	0	0	0	0	0	0	0	0	1	1
-------	---	---	---	---	---	---	---	---	---	---

1/2

for FA	F	A	F	A	F	A	F	A	F	A
--------	---	---	---	---	---	---	---	---	---	---

1/2


for FA	S	S	S	S	S	S	S	S	S	C
--------	---	---	---	---	---	---	---	---	---	---

REGISTER-C

Has the 2's
Complement.

FA	C	S
----	---	---

4(b)

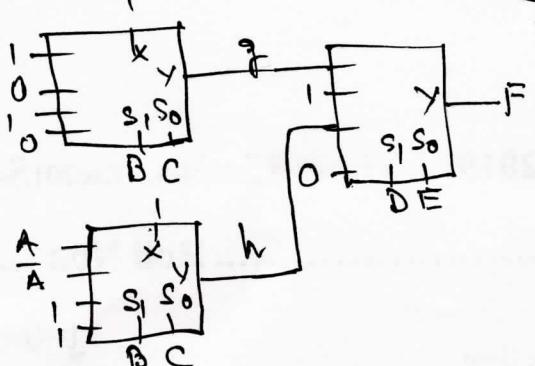

with
given
truth
table

C	B		ESc201A
S ₀	S ₁	Y	End
0	0	I ₀	Semester
0	1	I ₁	2019_20-I
1	0	I ₂	
1	1	I ₃	

With Given Truth
Table of MUX

$$g = 1 \cdot \bar{B}\bar{C} + 0 \cdot B\bar{C} + 1 \cdot \bar{B}C + 0 \cdot BC \\ = \bar{B}\bar{C} + \bar{B}C = \bar{B}(\bar{C} + C) = \bar{B}$$

1/2

$$h = A \cdot \bar{B}\bar{C} + \bar{A}B\bar{C} + 1 \cdot \bar{B}C + 1 \cdot BC \\ = A\bar{B}\bar{C} + \bar{A}B\bar{C} + C = [(A\bar{B} + \bar{A}B)\bar{C} + C] = (\bar{A}\bar{B} + \bar{A}B + C)$$

1/2

1/2

$$F = \bar{B}\bar{D}\bar{E} + 1 \cdot D\bar{E} + (\underbrace{\bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + C}_{(\bar{A}\bar{B} + \bar{A}B + C)})\bar{D}\bar{E} + 0 \cdot DE.$$

$$= \bar{B}\bar{D}\bar{E} + D\bar{E} + (\bar{A}\bar{B} + \bar{A}B + C)\bar{D}\bar{E}$$

$$= (\bar{B}\bar{D} + D)\bar{E} + (\bar{A}\bar{B} + \bar{A}B + C)\bar{D}\bar{E}$$

$$= (\bar{B} + D)\bar{E} + (\bar{A}\bar{B} + \bar{A}B + C)\bar{D}\bar{E}$$

$$= \bar{B}\bar{E} + D\bar{E} + A\bar{B}\bar{D}\bar{E} + \bar{A}B\bar{D}\bar{E} + C\bar{D}\bar{E}$$

$$\cancel{B}(\cancel{A}\bar{D}\bar{E} + \bar{E}) = A\bar{B}\bar{D} + \bar{B}\bar{E}$$

11

$$= \bar{B}\bar{E} + D\bar{E} + A\bar{B}\bar{D} + \bar{A}B\bar{D}\bar{E} + C\bar{D}\bar{E}$$

1/2 for each term correct

1/2 mark extra for doing what was instructed

4(b) Alternate more
Tedious method

		BC	DE	A = 0	A = 1
		00	01	11	10
		00	1 1	0 0	
		01	0 1	0 1	0 0
		11	0 0	0 0	0 0
		10	1 1	1 1	1 1

1/2

4(b) with the given Truth Table for MUX

1/2

A	B	C	D	E	F
X	0	0	0	0	1
X	1	0	0	0	0
X	0	1	0	0	1
X	1	1	0	0	0
X	X	X	1	0	1
1	0	0	0	1	1
0	0	0	0	1	0
1	1	0	0	1	0
0	1	0	0	1	1
X	0	1	0	1	1
X	1	1	0	1	1
X	X	X	1	1	0

$$F = \underbrace{D\bar{E}}_{x'z} + \underbrace{\bar{A}\bar{B}\bar{D}}_y + \underbrace{C\bar{D}E}_{z'z} + \underbrace{\bar{B}E}_{w'w}$$





$$\overbrace{\bar{A}\bar{B}\bar{D}E}^{u'}$$

1/2 for each term correct

4(b) with given
truth table.

1/2 mark extra for doing what was instructed

4(b)

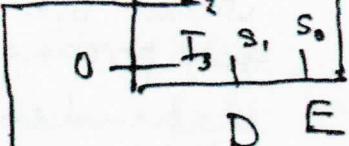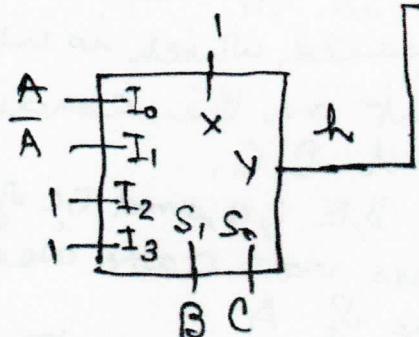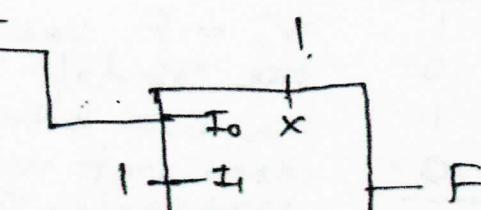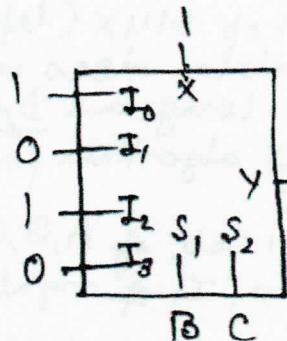

$$q = 1 \cdot \bar{B}\bar{C} + 0 \cdot \bar{B}C + 1 \cdot B\bar{C} + 0 \cdot BC$$

$$= \bar{B}\bar{C} + B\bar{C} = (\bar{B} + B)\bar{C} = \bar{C} \quad \text{by absorption theorem}$$

$$h = A \cdot \bar{B}\bar{C} + \bar{A}\bar{B}C + 1 \cdot B\bar{C} + 1 \cdot BC$$

$$= (A\bar{B} + B)\bar{C} + (\bar{A}\bar{B} + B)C =$$

$$= (A + B)\bar{C} + (\bar{A} + B)C \quad \text{by absorption theorem.}$$

$$= \bar{A}\bar{C} + B\bar{C} + \bar{A}C + BC \rightarrow A \oplus C + B \quad \text{1/2}$$

$$\rightarrow B(\bar{C} + C) = B$$

$$F = q \cdot \bar{D}\bar{E} + 1 \cdot \bar{D}E + h \cdot \bar{D}\bar{E} + 0 \cdot DE \quad \text{1/2}$$

$$= \bar{C}\bar{D}\bar{E} + \bar{D}E + (A \oplus C + B)\bar{D}\bar{E}$$

$$= \bar{D}(\bar{C}\bar{E} + E) + (A \oplus C + B)\bar{D}\bar{E}$$

$$= \bar{D}(\bar{C} + E) + (A \oplus C + B)\bar{D}\bar{E}$$

$$= \bar{C}\bar{D} + \bar{D}E + [(\bar{A}C + A\bar{C}) + B]\bar{D}\bar{E}$$

$$= \bar{C}\bar{D} + \bar{D}E + \bar{A}C\bar{D}\bar{E} + A\bar{C}DE + BDE$$

$$= \bar{C}(\bar{D} + (A\bar{E})D) + \bar{D}E + \bar{A}C\bar{D}\bar{E} + BDE$$

$$= \bar{C}(\bar{D} + A\bar{E}) + \bar{D}E + \bar{A}C\bar{D}\bar{E} + BDE$$

$$= \bar{C}\bar{D} + \bar{D}E + BDE + A\bar{C}\bar{E} + \bar{A}C\bar{D}\bar{E}$$



1/2 for each correct term

1/2
for
table

	A	B	C	D	E	F
x	0	0	0	0	1	✓
x	0	1	0	0	0	✓
x	1	0	0	0	1	✓
x	1	1	0	0	0	✓
	x	x	x	0	1	✓
1	0	0	1	0	1	✓
0	0	0	1	0	0	✓
1	0	1	1	0	0	✓
0	0	1	1	0	1	✓
	x	1	0	1	0	✓
x	1	1	1	0	1	✓
	x	x	x	1	1	✓

Now minimize F in terms of A, B, CDE \rightarrow 5 variables
needs 2 4×4 maps.

1/2 for
each
correct
entry of
K-Map.

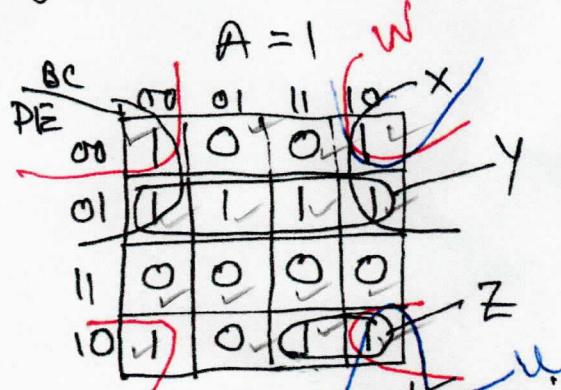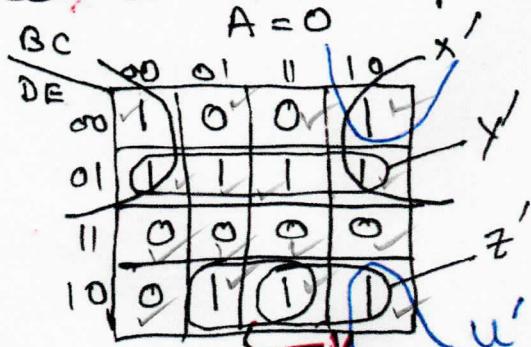

For $A = X$ same value enters the same location in both the maps.


1/2 for
each
term

$$F = \overline{CD} + \overline{DE} + B\overline{DE} + \overline{ACD}\overline{E} + \overline{ACE}$$

$\underbrace{\overline{CD}}$ $\underbrace{\overline{DE}}$ $\underbrace{B\overline{DE}}$ $\underbrace{\overline{ACD}\overline{E}}$ $\underbrace{\overline{ACE}}$

correct Compare with previous method is same

4(0)

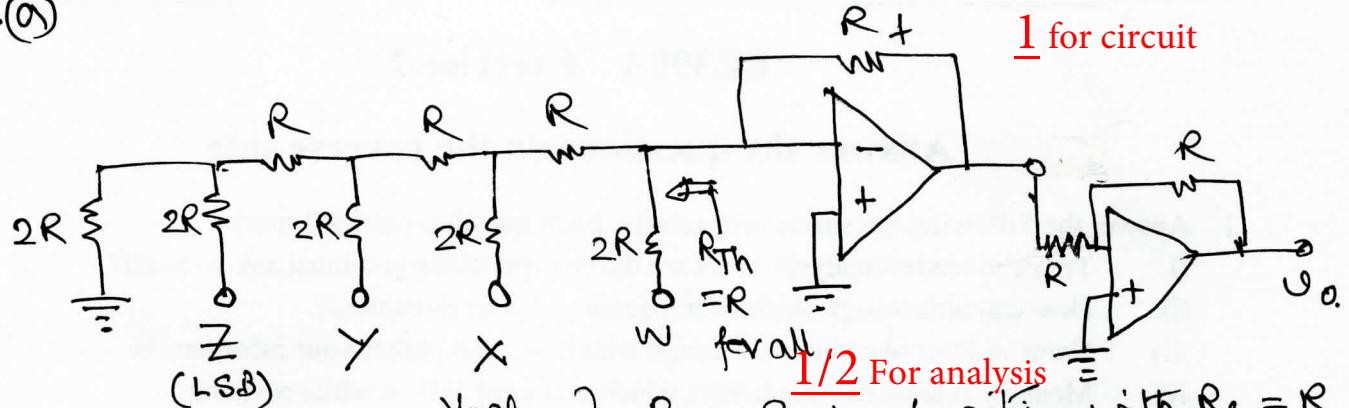

$$\begin{array}{l} w \times y \times z \\ 1000 \\ 0100 \\ 0010 \\ 0001 \end{array}$$

$$V_o = \frac{V_{ref}}{2}$$

$$V_o = \frac{V_{ref}}{4}$$

$$V_o = \frac{V_{ref}}{8}$$

$$V_o = \frac{V_{ref}}{16}$$


$R_f = R$ For $V_{ref} = 5V$, $V_o = 5 \left(\frac{W+X+Y+Z}{2} \right)$ 1/2 for each term

1/2 For analysis By Superposition with $R_f = R$

$$V_{o_{all}} = \frac{V_{ref}}{2} \left(W \times 2^0 + X \times 2^{-1} + Y \times 2^{-2} + Z \times 2^{-3} \right)$$

W, X, Y, Z can be 0 or 1.

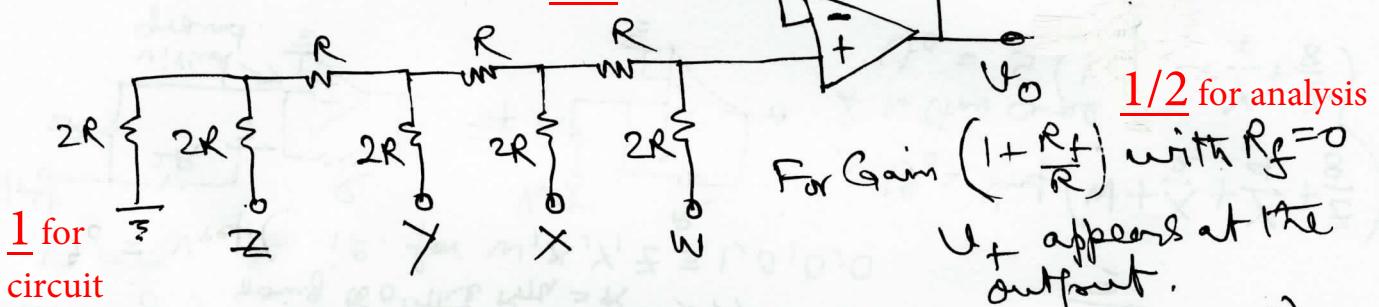With $R_f = 2R$, $V_o = V_{ref} \left(W + \frac{X}{2} + \frac{Y}{4} + \frac{Z}{8} \right)$



1/2 for analysis For Gain $(1 + \frac{R_f}{R})$ with $R_f = 0$

V_+ appears at the output.


$$\therefore V_o = \frac{V_{ref}}{2} \left(W \times 2^0 + X \times 2^{-1} + Y \times 2^{-2} + Z \times 2^{-3} \right).$$

$$V_o = N \cdot V_{REF} \sum_{i=0}^{N-1} \frac{B_i}{2^{N-i}}$$

$$V_{o_{all}} = \frac{V_{ref}}{2} \left(W + \frac{X}{2} + \frac{Y}{4} + \frac{Z}{8} \right)$$

For $V_{ref} = 5V$ $V_o = \frac{5}{2} \left(W + \frac{X}{2} + \frac{Y}{4} + \frac{Z}{8} \right)$

1/2 for each term

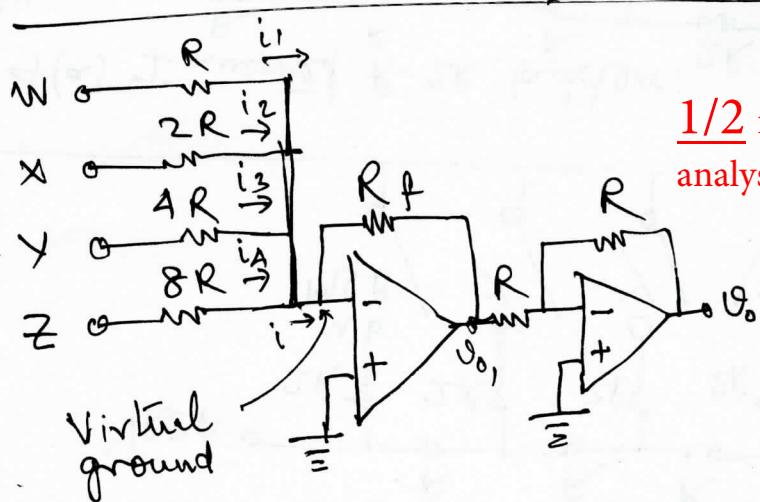

$$V_o = -i R_f$$

factor each term

$$= -R_f (i_1 + i_2 + i_3 + i_4)$$


$$= -R_f \left(\frac{W}{R} + \frac{X}{2R} + \frac{Y}{4R} + \frac{Z}{8R} \right) V_{ref}$$

$$= -\frac{R_f}{R} (W + \frac{X}{2} + \frac{Y}{4} + \frac{Z}{8}) V_{ref}$$

For $R_f = R$ & $V_{ref} = 5$


$$V_o = 5 \left(W + \frac{X}{2} + \frac{Y}{4} + \frac{Z}{8} \right)$$

1/2 for factor 1/2 for each term

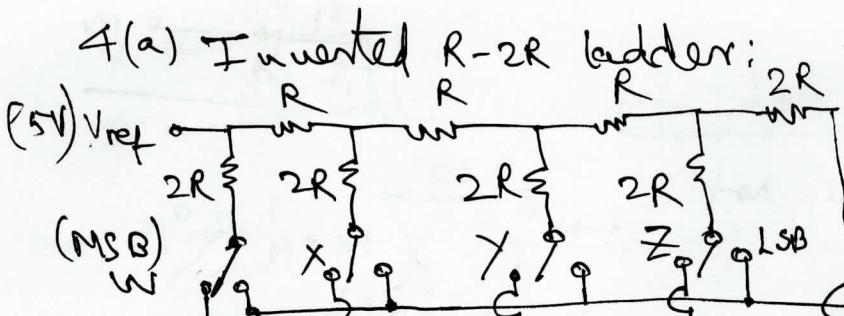


1 for circuit

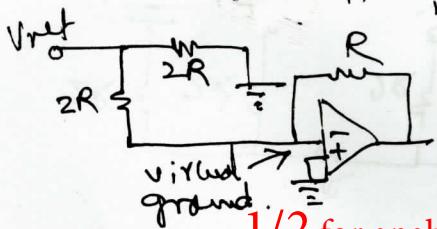Looking from the left going to 0 the $R_{Th} = R$
i.e. for $w, x, y, z \equiv 1, 0, 0, 0$



1/2 for analysis

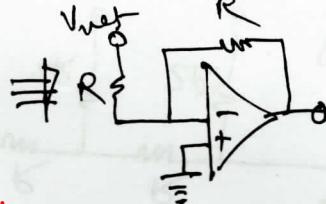

$$\therefore V_0 = V_{ref} \left(w + \frac{x}{2} + \frac{y}{4} + \frac{z}{8} \right)$$


& in this case

$$V_0 = 5 \left(w + \frac{x}{2} + \frac{y}{4} + \frac{z}{8} \right)$$

1/2 for 1/2 for each factor term

4(a) Consider an inverting amplifier with saturation voltages $\pm K V$. Since this is an inverting amplifier, with an input digital levels of $+5V$ it therefore requires another inverting amplifier of gain 1 with saturation voltages $\pm K V$.

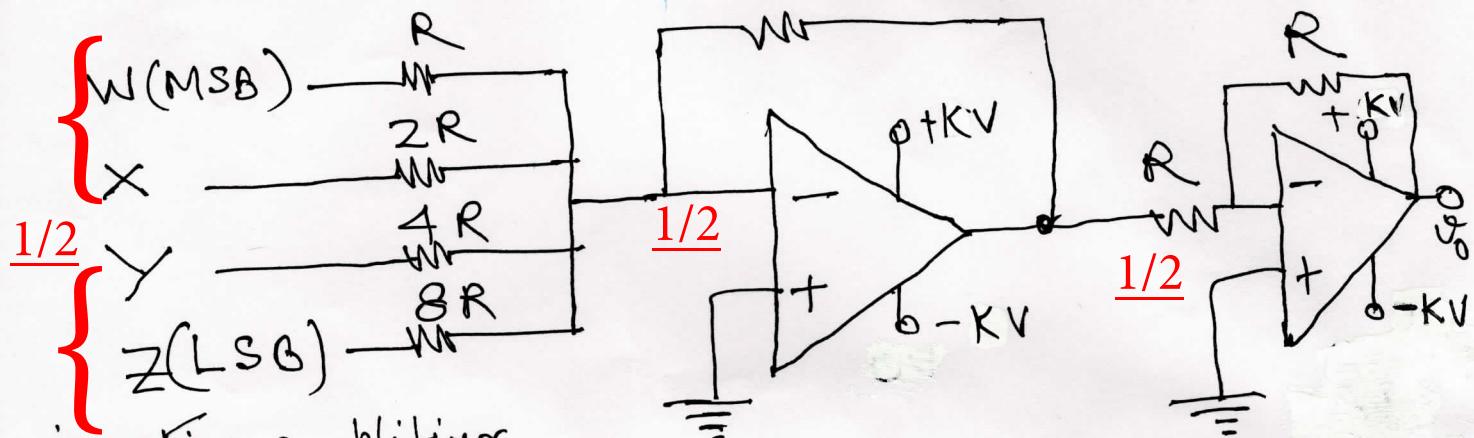Assuming that for the MSB the output is $+5V$, this input should have a gain of 1 for the 1st stage. Therefore the circuit is as shown below.



Inverting amplifier
gain for MSB = $-\frac{R}{R}$

$$\therefore V_o = -1 \times - \left[W(5V) \frac{R}{R} + X \times (5V) \frac{R}{2R} + Y \times (5V) \frac{R}{4R} + Z \times (5V) \frac{R}{8R} \right]$$

$$= \left(W + \frac{X}{2} + \frac{Y}{4} + \frac{Z}{8} \right) \times 5V \quad 1$$


Maximum value is $W, X, Y, Z = 1, 1, 1, 1$, or $V_o = 9.375V$

$\therefore K \geq 9.375V$, take $K = 10V$.


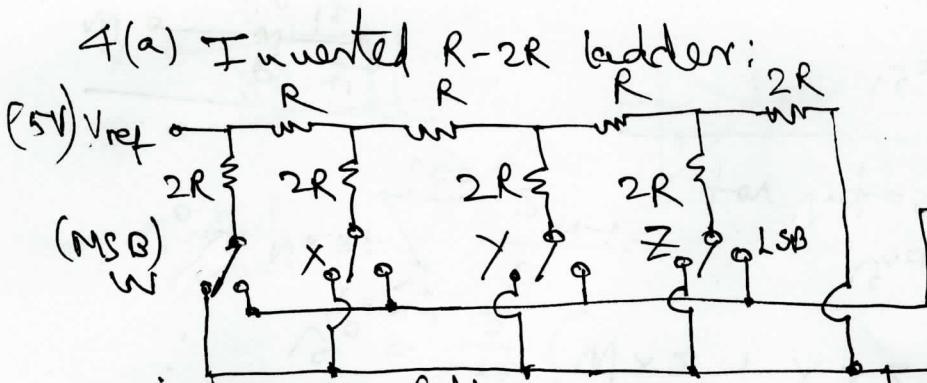
(b) Quantization error is given by the smallest change, which happens through the LSB.

$$\therefore \text{Quantization error} = \frac{1}{8} \times 5V = 0.625V \quad 1$$

There is a problem with the question as it states to take supply as $+5V$ and $0V$. This will not work. If someone shows that the Supply should be above $+9.375V$ and below $-9.375V$, then must be given and extra credit of 1.



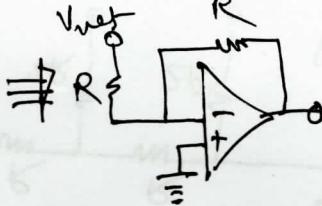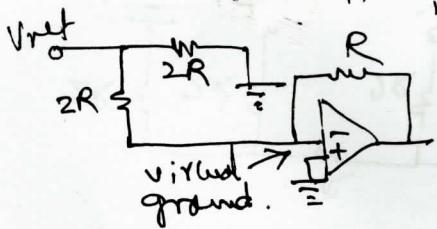Looking from the left going to 0 the $R_{Th} = R$
i.e. for $w, x, y, z \equiv 1, 0, 0, 0$




$$\therefore V_0 = V_{ref} \left(w + \frac{x}{2} + \frac{y}{4} + \frac{z}{8} \right)$$

& in this case

$$V_0 = 5 \left(w + \frac{x}{2} + \frac{y}{4} + \frac{z}{8} \right)$$

3) a)

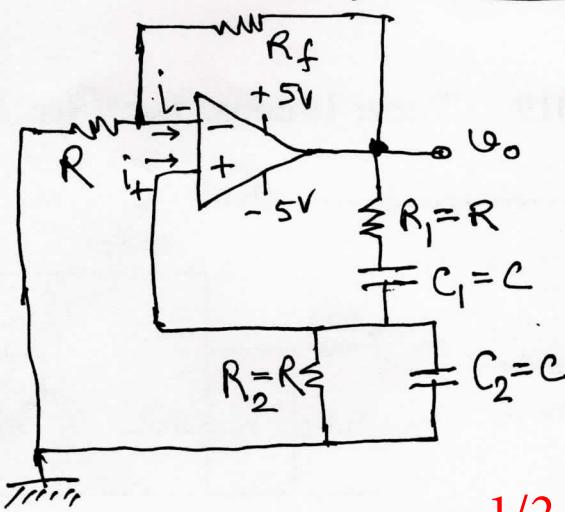

$$A_V V_+ = V_0$$

$$\frac{V_0 - V_-}{R_f} = \frac{V_- - 0}{R} \therefore i_- = 0$$

$$V_0 = R_f \left(\frac{1}{R_f} + \frac{1}{R} \right) V_-$$

$$= \left(1 + \frac{R_f}{R} \right) V_-$$

$$\approx \left(1 + \frac{R_f}{R} \right) V_+, \text{ Ideal Op-Amp.}$$

$$\therefore A_V = \left(1 + \frac{R_f}{R} \right) \quad \underline{1/2}$$

If someone shows this derivation, then an extra credit of 1/2 should be given.

$$\begin{aligned} \beta &= \frac{V_+}{V_0} = \frac{R_2 \parallel \frac{1}{j\omega C_2}}{R_1 + \frac{1}{j\omega C_1} + R_2 \parallel \frac{1}{j\omega C_2}} = \frac{R \parallel \frac{1}{j\omega C}}{R + \frac{1}{j\omega C} + R \parallel \frac{1}{j\omega C}} \quad \underline{1/2} \\ &= \frac{1}{R + \frac{1}{j\omega C}} + 1 = \frac{1}{1 + \frac{1 + j\omega RC}{j\omega C}} \\ &= \frac{1}{1 + \frac{(1 + j\omega RC)^2}{j\omega RC}} = \frac{1}{1 + 2 + \frac{1 + j^2\omega^2 R^2 C^2}{j\omega RC}} \end{aligned}$$

$$\underline{1} = \frac{1}{3 + j(\omega RC - \frac{1}{\omega RC})} \therefore A_V \beta = \left(1 + \frac{R_f}{R} \right) \frac{1}{3 + j(\omega RC - \frac{1}{\omega RC})} \quad \underline{1}$$

(b) { At resonance $\omega_0 RC - \frac{1}{\omega_0 RC} = 0$, $|A_V \beta|$ is maximum } $\underline{1/2}$

$$\text{or } \omega_0 = \frac{1}{RC}. \text{ For } \omega_0 = 100 \text{ kHz} \times 2\pi$$

$$\underline{1} \quad RC = \frac{1}{2\pi \times 10^5} [\text{s}] \Rightarrow \text{For } C = 318.3 \times 10^{-12} \text{ F}$$

$$R = \frac{1}{2\pi \times 10^5 \times 318.3 \times 10^{-12}} = 5000.16 \Omega \approx 5 \text{ k}\Omega \quad \underline{1}$$

(c) For stable oscillation at resonance $|A_V \beta| \geq \frac{1 + R_f/R}{3}$ $\underline{1}$

$$\text{& for } |A_V \beta| \geq 1; \frac{R_f}{R} \geq 2 \quad \text{or } R_f \geq 2R = 10 \text{ k}\Omega \quad \underline{1}$$

$$\therefore R_f = \underline{\underline{(10+8) \text{ k}\Omega}}$$

δ is a very small number.

Full marks even if one does not mention about Delta.

2) a) At $t=0^-$, $V_- = -4.9V$ and since sufficient time has lapsed no current is flowing through the resistance 'R'. $\therefore V_+ = 0V$. 1

The infinite open loop comparator will send the output V_o to saturation level. But when V_o crosses the voltage of the Zener it is clamped at the voltage ($V_Z + V_{on}$). Since $V_{on} = 0$, $V_{o,t=0^-} = V_Z = +9V$. 1

(b) Since the input pulse is only for a short while ($0.1ms$), C_{in} acts as d.c. blocking and an a.c. short. 1/2

Since at $t=0^+$, V_+ is still at $0V$ and V_- has become positive, $(5 - 4.9) = +0.1V$, the comparator will switch to the negative saturation value. However, one of the Zeners work now and the voltage V_o will be clamped at $-V_Z = -9V$.
 $\therefore V_{o,t=0^+} = -9V$. 1.5

(c) Question is that when the input pulse is gone, what is the voltage V_+ or V_o ?

As the capacitor 'C' has been charged to a voltage of $+9V$ and its right terminal is at $-9V$, $V_+ = -18V$. 1


$\therefore V_o$ will continue to remain at $-9V$ till V_+ reaches $V_- = -4.9V$. 1

Note that the diode is reverse biased and will not conduct.

$\therefore V_+$ will leak through R with a time constant $RC = T$ where it is assumed that $V_+(\infty) = 0$.

$$\therefore \underline{V_+ = -18 e^{-t/T}}$$

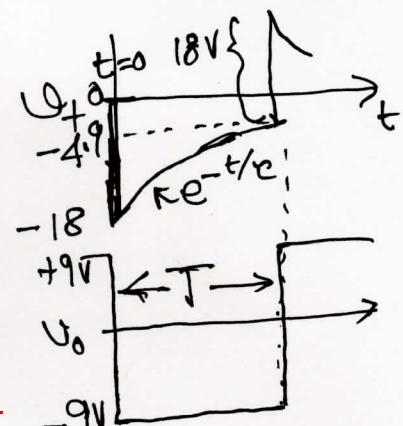\therefore The time till which V_o holds at $-9V$ is T , the time till V_+ reaches $-4.9V$, or $-4.9 = -18 e^{-t/T}$ or $T = RC \ln(\frac{18}{4.9})$
 For $R = 4k\Omega$, $C = 2\mu F$, $RC = 8ms$ $\therefore T = 8ms \times 1.3(s) = 10.4ms$ 1



1) (a) In the base-emitter loop: assume $V_{BE\text{active}} = 0.7 \text{ V}$

$$5 \text{ V} = I_B \times 10 \text{k}\Omega + 0.7 \text{ V} + I_E \times 1 \text{k}\Omega \quad \underline{1/2}$$

$$\text{or } 4.3 = 10I_B(k) + (89+1)I_B(k) \Rightarrow I_B = \frac{4.3}{100} \text{ mA}$$


$$\text{or } I_B = 43 \mu\text{A} \quad \underline{1}$$

$$\therefore I_C = \beta_F I_B = 89 \times 43 \mu\text{A} = 3.827 \text{ mA} \quad \underline{1/2}$$

check for active region $V_C = -3.827 \text{ V} + 5 = 1.173 \text{ V}$, $V_B = -0.43 \text{ V}$. \therefore Base reverse biased.

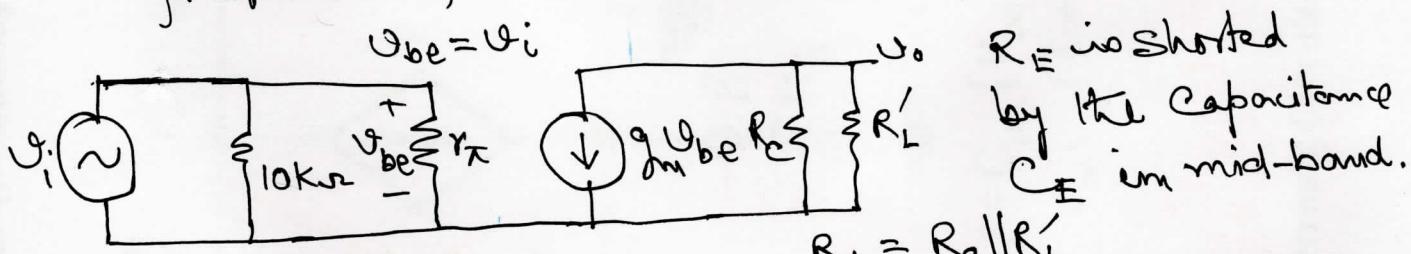(b) Assuming C_{in} and C_{out} are short at all

frequencies, the a.c. equivalent circuit is:



$$g_m = \frac{I_C}{V_T} = \frac{3.827}{26}$$

$$= 147.2 \text{ mS} \quad \underline{1}$$

$$\therefore A_{V\text{mid}} = \frac{V_o}{V_i} = \frac{V_o}{V_{be}} = - \frac{g_m R_L}{V_{be}} = -147.2 \times 0.91$$

$$= -133.95 \approx -134. \quad \underline{1}$$

$$(c) f_{L3dB} = \frac{1}{2\pi C_E}, \quad C_E = R_C F_m \quad \underline{1/2} \oplus \text{No contribution}$$

$$R_C = R_E // r_e \quad \boxed{\text{as } V_i = 0 \text{ for calculation and therefore the base would be grounded}}$$

$$r_e = \frac{N_T}{I_C} = 6.794 \Omega \quad \therefore R_E // r_e = R_C F_m = \frac{1000 \times 6.794}{1006.794} = 6.748 \Omega \quad \underline{1/2}$$


$$\therefore C_E \approx 6.75 \Omega \times 10 \times 10^{-6} \text{ F} = 67.5 \mu\text{s} \quad \underline{1/2}$$

$$\therefore f_{L3dB} = \frac{1}{2\pi 67.5 \mu\text{s}} = 2.36 \text{ kHz} \quad \underline{1/2}$$

$$f_{H3dB} = \frac{C_{in}}{C_{in} + C_{\mu\pi}} = \frac{C_{\mu\pi}}{C_{\mu\pi} + C_{in}} = \frac{C_{\mu\pi}(1 + g_m R_L)}{C_{\mu\pi} + C_{\mu\pi}(1 + g_m R_L)} = 5 \text{ pF} (1 + 134)$$

$$= 675 \text{ pF} \quad \underline{1/2}$$
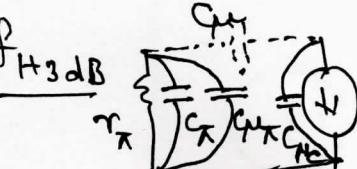
$$C_{\mu\pi} = C_{\mu\pi} \left(1 + \frac{1}{g_m R_L}\right) = C_{\mu\pi} \left(1 + \frac{1}{134}\right)$$



$$C_{in} = C_{\mu\pi} + C_{\mu\pi} = 725 \text{ pF} \quad \underline{1/2}$$

$\therefore C_{in} = C_{\mu\pi} + C_{\mu\pi} = 725 \text{ pF}$ $\therefore f_{H3dB} = \frac{1}{2\pi \times 0} = \underline{1/2} \oplus (\text{No})$

$$\therefore f_{H3dB} = \frac{1}{2\pi \times 0} = \underline{1/2} \oplus (\text{No})$$

$$\text{or } C_{in} = 0 \quad \text{Now } C_{in} \text{ cannot be neglected. } C_{in} \approx 5 \text{ pF} \times 0.91 \text{ k} \Omega \text{ or } f_{H3dB} = 35 \text{ GHz}$$

$C(\mu/\text{c})$, which was unimportant now becomes dominant. Whoever shows this gets an extra mark of 1.