

Closed Book, Notes, & Mobiles. Put your Name, Roll No. & Section on all attached sheets. There are Eight questions for a total of 70 marks. Credit for each question is indicated on the left-hand margin. Show all necessary calculations. Best wishes for an excellent performance.

1. The RC coupled amplifier of fig. 1 is biased to operate in the forward active region. Assume C_{in} and C_{out} to be very large.

- [2] (a) Find the collector bias current (I_C) for $\beta_F = 89$.
 [3] (b) Calculate the Mid-band Voltage Gain ($A_{v1} = v_{o1}/v_i$).
 [4] (c) If $C_E = 10\mu f$, the base-emitter junction capacitance $C_{\pi} = 50pf$, and the Base-collector capacitance $C_{\mu} = 5pf$, estimate the high and the low 3dB cutoff frequencies.

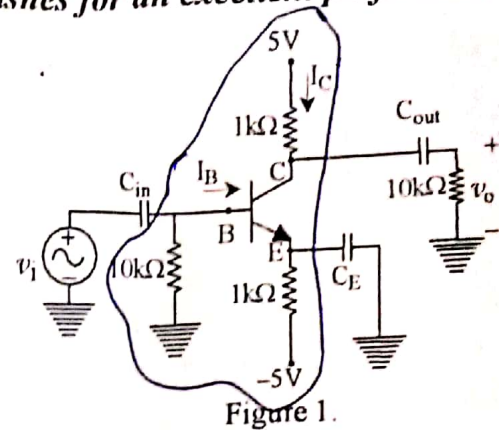


Figure 1.

2. For the circuit shown in fig. 2, assume that all the diodes have $V_{on} = 0$ and the OpAmp to be ideal.

Assume C_{in} to be very large. The circuit has been sitting idle for a long time and a 5V pulse appears at the input only at $t = 0^+$. (Remember that the voltage across a capacitor cannot change instantaneously)

- [2] (a) What are the voltages v_+ (at non-inverting input of OpAmp) and v_o (output) at $t = 0^-$?
 [3] (b) At $t = 0^+$, a 5V, 0.1ms pulse appears at the input. Find the output voltage v_o at $t = 0^+$.
 [4] (c) If $R = 4k\Omega$ and $C = 2\mu F$, calculate the time for which the output voltage holds at the result found in (b) above.

 


Figure 2.

3. The circuit shown in fig. 3 is supposed to oscillate sinusoidally at a frequency of 100 kHz.

- [3] (a) Derive an expression for the closed loop gain $A_{v\beta}$ for the ideal OpAmp, where A_v is the non-inverting voltage gain and β is the positive feedback fraction (v_+/v_o).
 [3] (b) If the given capacitance $C = 318.3pF$, find the required value of R . Derive any expression that you need to use for the calculation.
 [3] (c) For stable oscillation, find the required value of R_f .

 



Figure 3.

- [4] 4(a) A 4-bit digital input ($W\{MSB\}$, X , Y , and $Z\{LSB\}$) has voltage levels +5V as '1' and 0V as '0', respectively. Construct and sketch a Digital-to-Analog Converter (DAC) using an ideal OpAmp, powered by a +5V supply and the other supply input grounded. You may use resistances R , $2R$, $4R$, ..., etc. along with the OpAmp. Derive an expression for the analog output voltage (v_o) as a function of the digital inputs. What is the quantization error (%) in the conversion?


ANSWERS/SCRIPTS WILL BE SHOWN at 11:15-12:15 AM on Nov. 23, 2019 (Saturday) in your respective Tutorial Rooms, EXCEPT for Section W2 which will be in Rm. T207 instead of T112.

PTO

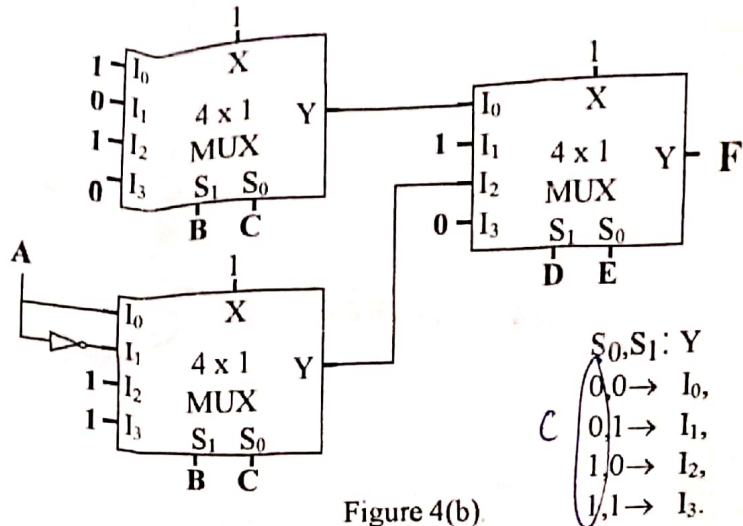
- 4(b) F is a Boolean function of the Boolean variables A, B, C, D, & E, as shown in fig. 4(b). Find the Boolean expression of F(A, B, C, D, E) in its minimum Sum of Products (SOP) form. X is the enable input set at 1.



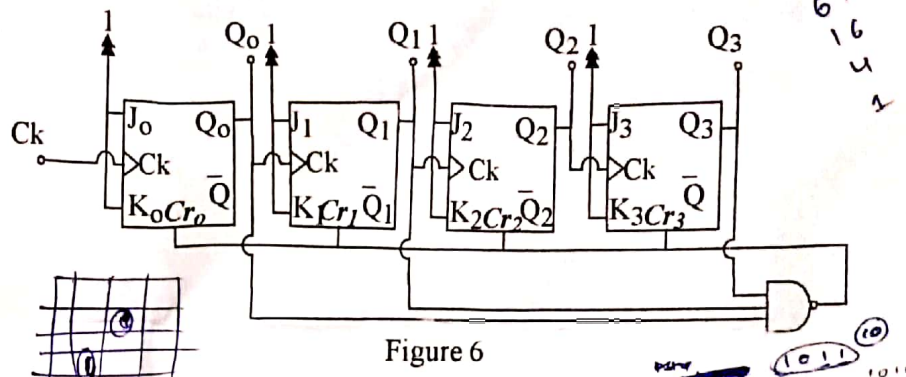5. Two numbers 85.125 and 32.5 are stored in 10-bit (7+3) binary registers with the 3 bits after the decimal point.
- [3.5] (a) Show the two registers with the two binary numbers equivalent to 85.125 and 32.5.
- [3.5] (b) Show the process of subtraction of the smaller number from that of the larger (show how smaller decided) using 2'-complement method.
- [2] (c) Using any extra number of 10-bit registers required, show the implementation of obtaining the 2'-complement from the required register in (a), using gates and full-adders.



- [8] 6. A Ripple counter, shown in fig. 6, works on the negative edge of the clock. Sketch the clock (Ck) and the Q_0 , Q_1 , Q_2 , Q_3 output pulses on the same time scale and hence write the sequence of states of the counter. The $Clear(Cr)=0$ sets a Flip-Flop to $Q=0$, $\bar{Q}=1$ state for $Preset(P_r)=1$ (assumed here to be always set at this value). $Cr=1$ has no effect for $P_r=1$. If this counter, has a count of N, what is N?
7. A Binary Coded Decimal (BCD) {A(MSB), B, C, and D(LSB)} input is to be displayed on the seven-segment display, shown in fig. 7. However, when the numbers 0, 3, 7, 8, and 9 appear, then only the number is to be displayed. For the other numbers, an inverted-C { \square (a, b, c, and d to be illuminated) } is to be displayed.
- [9] Establish the **combinational logic** and **logical voltages** (1 or 0) that are required to be connected to the segments a, b, c, d, e, f, and g, such that the above mentioned constrained-display can be realized with a **minimum number of gates**. No Circuit Diagram is needed.
8. A modulo-6 synchronous counter is to be designed with J-K flip-flops. The counter should start at 000.
- [6] (a) From the J-K flip-flop truth table given on the right develop and sketch a clean circuit for the same with minimum number of J-K flip-flops and other gates.
- [3] (b) This counter is to be converted to a **modulo-12 counter** using one extra T-Flip-Flop to this modulo-6 counter. Show the modification of this circuit required. The truth table for the T-Flip-Flop is obtained from the J-K truth table using $J=K=1$.

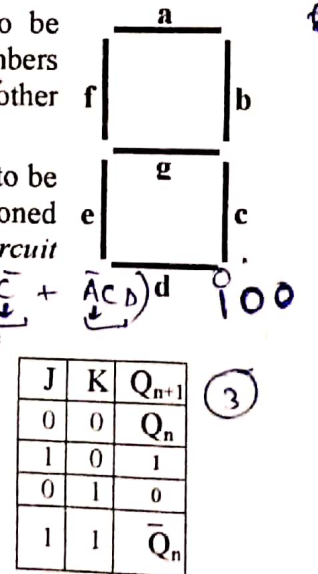

J	K	Q_{n+1}
0	0	Q_n
1	0	1
0	1	0
1	1	\bar{Q}_n

ANSWERS/SCRIPTS WILL BE SHOWN at 11:15-12:15 AM on Nov. 23, 2019 (Saturday) in your respective Tutorial Rooms, EXCEPT for Section W2 which will be in Rm. T207 instead of T112.

$$(A + \bar{B} + \bar{C} + \bar{D}) \cdot (\bar{A} + B + C + \bar{D}) \text{ PTO}$$

$$F = \bar{A} \bar{B} \bar{C} \bar{D} + A \bar{B} \bar{C} \bar{D} + \bar{A} \bar{B} \bar{C} \bar{D} + A \bar{B} \bar{C} \bar{D}$$