


## Major Quiz-2

Duration: 45 min.

Max Marks: 15

1. Consider the circuit alongside with  $V = 10\angle 0^\circ V$  and the impedances corresponding to the elements given as:  $R_1 = 4\Omega$ ,  $R_2 = 8\Omega$ ,  $Z_C = -j6\Omega$  and  $Z_L = j5\Omega$ .

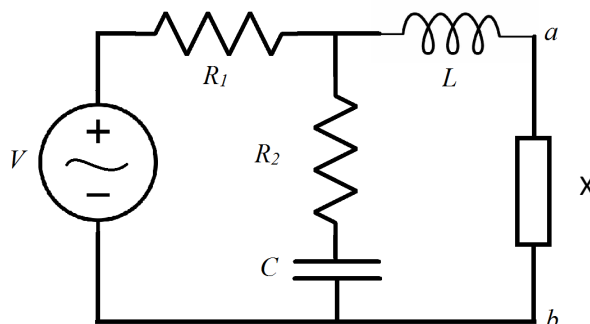
(a) Calculate the Thevenin equivalent as observed by the load, X. [3]



**Solution:**

Short voltage source to find  $Z_{Th}$ :


[1.5 marks]

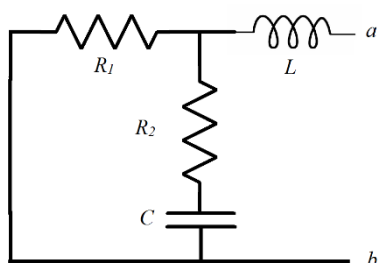

$$Z_{Th} = j5 + 4 \parallel (8 - j6) = j5 + \frac{4(8 - j6)}{4 + 8 - j6} = 2.933 + j4.467 \Omega = 5.344\angle 56.71^\circ \Omega$$

To find  $V_{Th}$ :

[1.5 marks]

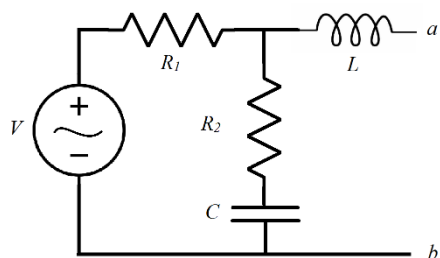

$$V_{ab} = V_{Th} = \frac{8 - j6}{4 + 8 - j6} 10V = 49.193 - j8.944V = 7.454\angle -10.3^\circ V$$

(b) Determine the load impedance,  $Z_X$ , that maximizes the average power drawn from the circuit. What is the maximum average power drawn by the load? [3]

**Solution:**

Load impedance for maximum average power:

[1 mark]


$$Z_L = Z_{Th}^* = 2.933 - j4.467 \Omega$$

Maximum average power:

[1 mark]

$$P_{max} = \frac{|V_{Th}|^2}{8\text{Re}(Z_{Th})} = \frac{(7.454)^2}{8(2.933)} = 2.368 W$$

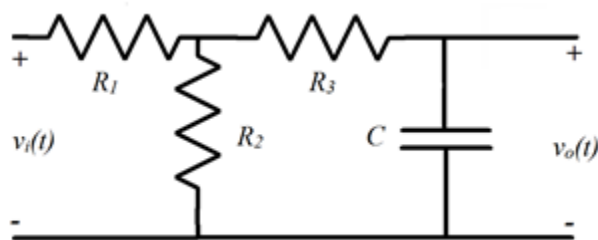2. Consider the circuit given below, with  $R_1 = 2k\Omega$ ,  $R_2 = 2k\Omega$ ,  $R_3 = 1k\Omega$  and  $C = 10\mu F$ .



(a) Calculate the transfer function,  $H = \frac{v_o}{v_i}$  [3]

**Solution:** Using potential divider

[2 marks for  $H(\omega)$ ]

$$v_o = \frac{1/j\omega C}{R_3 + 1/j\omega C} \times \frac{R_2 || (R_3 + 1/j\omega C)}{R_1 + R_2 || (R_3 + 1/j\omega C)} v_i = \frac{v_i}{2(1 + 2000j\omega C)}$$

$$H(\omega) = \frac{v_o}{v_i} = \frac{0.5}{1 + j\frac{\omega}{\omega_0}};$$

$$\omega_0 = \frac{1}{2000C} = 50 \text{ rad/s}$$


[1 mark for  $\omega_0$ ]

(b) Plot the Bode magnitude plot for the transfer function derived in (a). What sort of a filter does this circuit act as? [3]

**Solution:**

$$20\log(|H|) = 20\log(0.5) - 20\log\left(\sqrt{1 + \left(\frac{\omega}{50}\right)^2}\right) \text{ dB}$$

$$20\log(|H|) = \begin{cases} -6.02 \text{ dB}; & \text{for } \omega \ll 50 \text{ rad/s} \\ -6.02 \text{ dB} - 20\log\left(\frac{\omega}{50}\right) \text{ dB}; & \text{for } \omega \gg 50 \text{ rad/s} \end{cases}$$

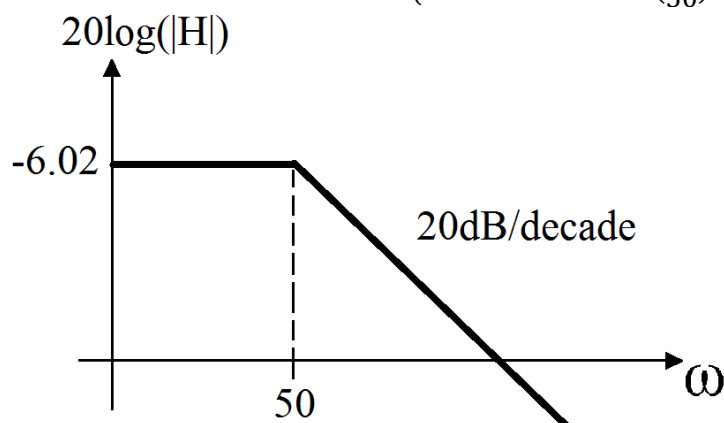


[2 marks for plot]

Represents a **low-pass** filter

[1 mark]

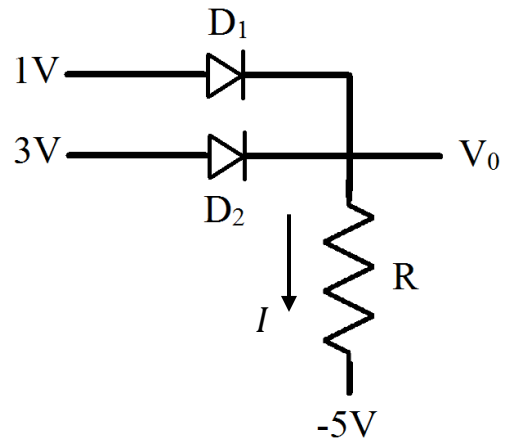**3. For the circuit shown below, calculate  $I$  and  $V_0$ , if  $R = 1k\Omega$ . Assume that the diodes are ideal. [3]**



**Solution:**

**Case 1:** if both diodes are on:

In this case,  $V_0 = 1V$  and  $V_0 = 3V$ ; which is not possible.

⇒ Initial assumption is incorrect

**Case 2:** if both diodes are cut-off:

In this case,  $V_0 = -5V$  which is less than both  $1V$  and  $3V$  implying that both diodes must be on.

⇒ Contradiction ⇒ Initial assumption is incorrect

**Case 3:** if  $D_1$  is on while  $D_2$  is off:

$V_0 = 1V \Rightarrow$  voltage across  $D_2$   $2V$  (forward bias)  $\Rightarrow D_2$  is on; which contradicts the initial assumption

⇒ Initial assumption is incorrect

**Case 4:** if  $D_2$  is on and  $D_1$  is off:

$V_0 = 3V$  voltage across  $D_1$  is  $-2V \Rightarrow D_1$  is off which satisfies the initial condition.

[1 mark]

Therefore,

$$I = \frac{(3 - (-5))V}{1k\Omega} = 8mA \text{ and } V_0 = 3V$$

[1 mark+1 mark]